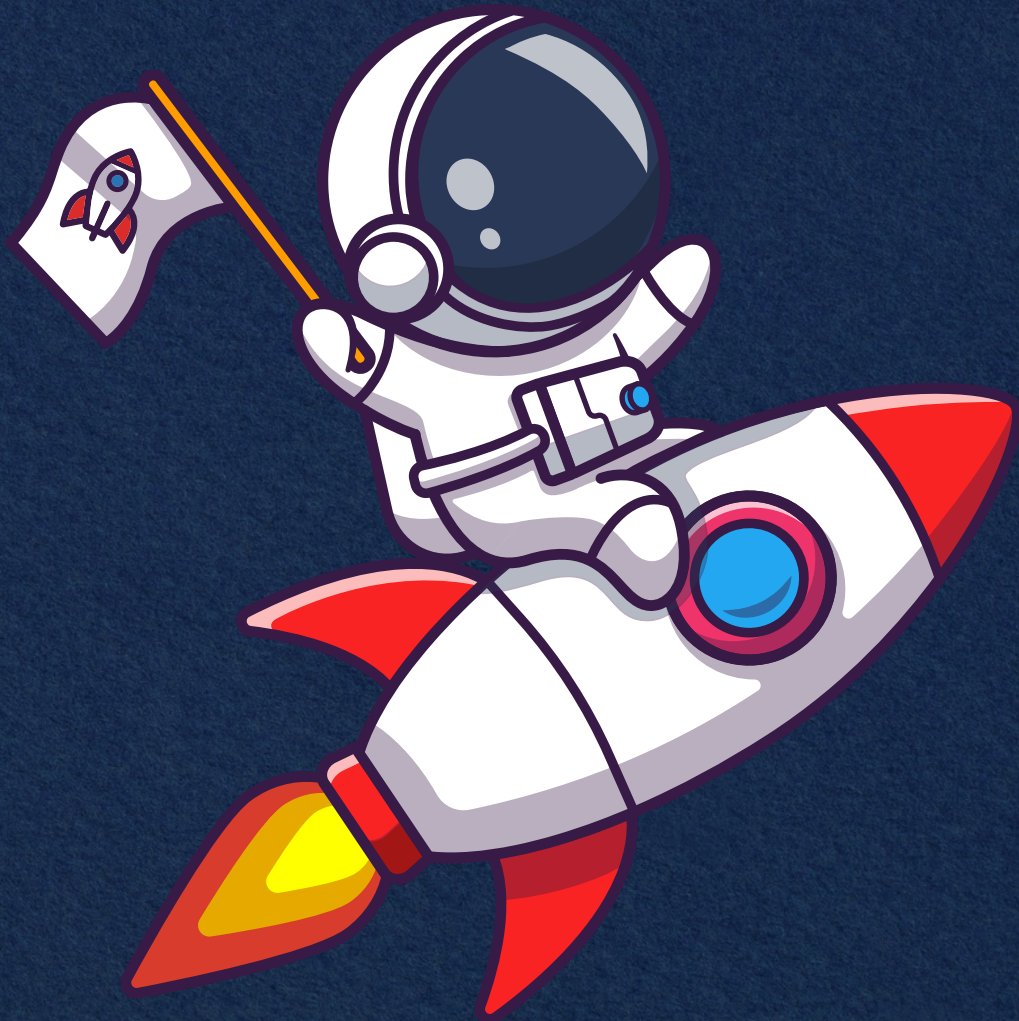


Class 12



PHYSICS

SHORT NOTES



Chapter - 3

Current Electricity

★ Electric current :- Net electric charge flowing per unit time through an area of cross section.

$$I = \frac{\text{No. of charges}}{\text{time}} = \frac{Q}{t}$$

→ Unit :- Ampere or Coulomb
Sec.

→ Dimensional :- $[M^0 L^0 T^{-1} A^1]$

★ Average current :- $\frac{\Delta q}{\Delta t} = \frac{q_2 - q_1}{t_2 - t_1}$

★ Instantaneous Current :- total current at any instant

$$I_{\text{int}} = \frac{dq}{dt}$$

→ Scalar or tensor quantity.

E.g. $I = I_1 + I_2$

★ Electric Current in conductor :-

Case - I :- When external electric field is not applied then,

$$\vec{u}_{\text{avg}} = \frac{\vec{u}_1 + \vec{u}_2 + \dots + \vec{u}_n}{n} = 0$$

→ Average velocity of e^- is zero but avg. speed of e^- is not zero.

Case - II :- When battery is applied :-


$$a_e = \frac{eE}{m_e}$$

★ Ohm's Law:-

$$V = RI$$

→ Resistance depend on nature and dimension of conductor not on V & I .

→ Unit of R :- Ω (ohm)

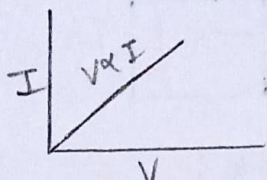

• factors on which Resistance depends:-

① length ($R \propto l$)

② cross sectional area of wire ($R \propto \frac{l}{A}$)

③ Temperature (T)

Conductor $\rightarrow T \uparrow R \uparrow$
Semiconductor $\rightarrow T \uparrow R \downarrow$
Alloy $\rightarrow T \uparrow, R \rightarrow$ No change

④ Nature of Material (Resistivity)
($Ag < Cu < Al < Fe$)

★ Note:-

$$R = \rho \frac{l}{A}$$

$$V = I \rho \frac{l}{A}$$

where ρ = Resistivity

★ Current Density :- current flowing through conductor in per unit area.

$$J = \frac{I}{A}$$

→ Unit $\rightarrow$ Ampere/ m^2

→ It is vector quantity

→ Dimensional :- $[M^0 L^{-2} T^0 A^1]$

→ Direction of current ~~is~~ density is in direction of current.

$$I = \vec{J} \cdot \vec{A}$$


★ Note :-

$$\boxed{J = \sigma E}$$

$$\boxed{\vec{J} = \vec{E} \cdot \sigma}$$

$$\boxed{\sigma = \frac{1}{\rho}}$$

→ for conductors :-

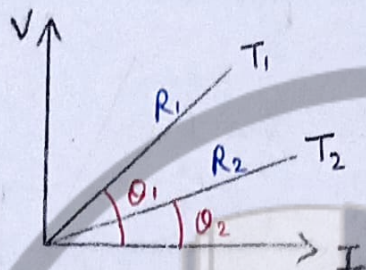

If $T_1 > T_2$ then $\theta_1 > \theta_2$ & $R_1 > R_2$

★ Drift Velocity :- average velocity of free electrons inside a conductor when external electric field is applied across the conductor.

Vector form :-

$$\boxed{\vec{V}_d = \left(\frac{e\vec{E}}{M} \right) \tau}$$

where τ = Relaxation time.

Scalar form :-

$$\boxed{V_d = \frac{eET}{M}}$$

$\tau = 10^{-14}$ sec.

→ Drift velocity of e^- is always opposite to direction of $\vec{E}$.

★ Mobility :-

$$\boxed{\mu = \frac{V_d}{E} = \frac{e\tau}{M}}$$

→ Unit :- $\frac{Csec}{Kg}$ or $\frac{m^2}{Vs}$

★ Relation b/w drift velocity and current :-

$$\boxed{I = V_d enA} \text{ or } \boxed{I = neAV}$$

★ Note:-

Resistivity: $\rho = \frac{M}{e^2 \tau M}$

- ① Drift velocity depend on e^- per unit volume.
- ② $E=0$, then path of electrons is straight.

★ Limitations of Ohm's law :-

- not apply to non-ohmic devices like diodes & transistors.
- It fails for material where resistance varies with temperature.
- Ohm's law is invalid for electrolytic solutions.

★ Electrical Resistivity:-

- It is equal to resistance of material when length is 1 meter and cross sectional area is 1m^2 .

So, $\rho = R$ at length = 1 m, area = 1m^2

→ Unit:- ohm-meter (Ωm)

$$\rho = \frac{M}{ne^2 \tau}$$

→ Resistivity depends on:-

- ① $\rho \propto \frac{1}{n}$
- ② $\rho \propto \frac{1}{\tau}$

★ Concept:- (Effect of temperature)

① for conductors:-

Temperature $\uparrow \rightarrow$ no. of vibration $\uparrow \rightarrow \tau \downarrow$ (more effective)

On $T \uparrow$, $e \uparrow$

② for semiconductors:-

Temperature $\uparrow \rightarrow$ no. of free $e^- \uparrow$ (n) (more effective)

On $T \uparrow$, $\rho \downarrow$


★ Variation of Resistance / Resistivity with Temperature :-

① for Conductors :-

$$R_T = R_0 (1 + \alpha \Delta T)$$

$$\rho_T = \rho_0 (1 + \alpha \Delta T)$$


where α is thermal coefficient

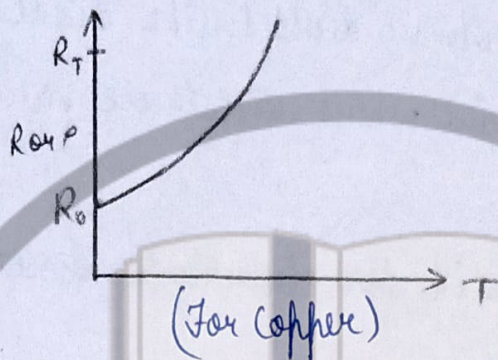

② for Semiconductors :-


$$R_T = R_0 (1 - \alpha \Delta T)$$
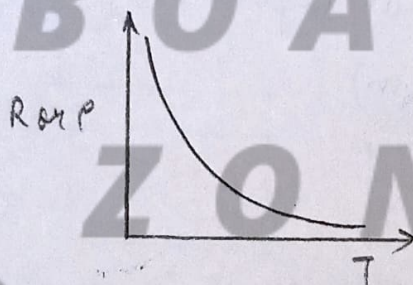
$$\rho_T = \rho_0 (1 - \alpha \Delta T)$$



③ for Alloys :-

$$R_T = R_0$$

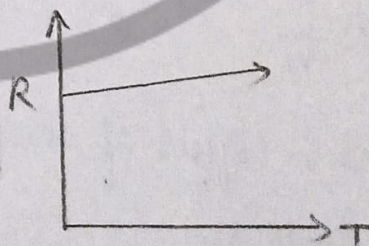

★ Note :-

For conductor, $\alpha = +ve$

for semiconductor, $\alpha = -ve$

for alloy, $\alpha = 0$

* Electric Power & Energy:- Dissipated energy per unit time is called electrical Power.

$$\Delta W = E = VI\Delta t$$

$$P = \frac{\Delta W}{\Delta t} = VI$$

$$P = I^2 R = \frac{V^2}{R}$$

→ Unit of Power → Watt (W)

→ Unit of Energy → Joule

→ Commercial unit of electrical energy → kWh (Kilo watt hour)

* Combination of Resistors:-

1. Series Combination:-

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = nR \quad (\text{For same resistors})$$

② Parallel Combination:-

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{R}{n} \quad (\text{For same resistors})$$

* Cell:- Convert chemical energy into electrical energy

→ Cell produce potential difference across terminals which forces the electrons to move.

→ Combination of more than one cell called battery.

★ Electromotive force (E.M.F):- maximum potential difference across the e^- of cell when no current drawn from it.

$$\boxed{\mathcal{E} = I(R + r)}$$

→ unit → Volt (V), $J C^{-1}$

→ It is applicable for open circuit only.

★ Internal Resistance :- Resistance offered by electrolyte and electrode of cell when electric current flows through it.

→ Internal resistance depends on:-

- Distance by electrodes
- Nature, Concentration & temp. of electrolyte
- Nature of electrodes.

→ Due to internal resistance, potential across terminals decreases.


★ Terminal Potential Difference :- (V) When current flows through the circuit then potential difference is called terminal voltage.

$$\boxed{V < \mathcal{E}}$$

$$\boxed{V = \mathcal{E} - Ir}$$


★ Note :-

① During Discharging ($V < \mathcal{E}$)

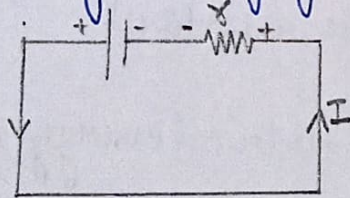


$$\boxed{V = \mathcal{E} - Ir}$$

(Open Circuit)

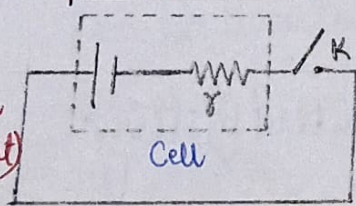


Emf is measured

② During Charging ($V > \mathcal{E}$)

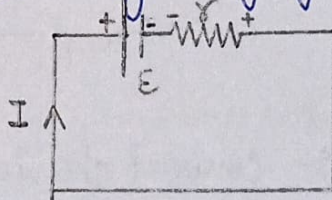

$$\boxed{V = \mathcal{E} + Ir}$$

(Closed Circuit)

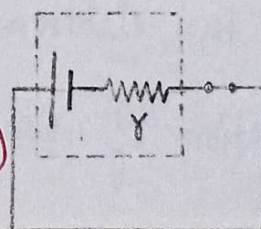

Potential difference is measured

A. Internal Resistance of a Cell in terms of $\mathcal{E}$, V & R :-

$$r = \frac{\mathcal{E} - V}{I}$$

$$r = \left(\frac{\mathcal{E}}{V} - 1 \right) R$$

A. Combination of Cell :-

1. Series Combination :-

$$V = \mathcal{E}_{eq} - I r_{eq}$$

$$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2$$

$$r_{eq} = r_1 + r_2$$

Case :- If there are n no. of same cells


$$\mathcal{E}_{eq} = n\mathcal{E}$$

$$r_{eq} = nr$$


$$I = \frac{\mathcal{E}_{eq}}{R + r_{eq}} = \frac{n\mathcal{E}}{R + nr}$$

A. Note :-


① If Polarity of cell is different.

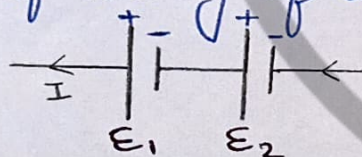
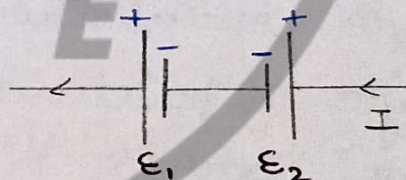
$$\mathcal{E} = \mathcal{E}_1 + \mathcal{E}_2$$


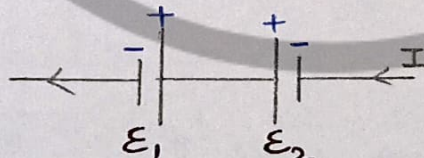
$$\mathcal{E} = \mathcal{E}_1 - \mathcal{E}_2$$



$$\mathcal{E} = \mathcal{E}_2 - \mathcal{E}_1$$

But $r_1 + r_2 = r$ for all conditions.

② Internal Resistance of ideal cell is zero.

2. Parallel Combination :-

$$V = \left(\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2} \right) r_p - I r_p$$

$$\varepsilon_{eq} = \left(\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2} \right) r_p$$

$$r_{eq} = r_p = \left(\frac{1}{\frac{1}{r_1} + \frac{1}{r_2}} \right)$$

Case :- If there are n number of same cells.

$$\varepsilon_{eq} = \varepsilon$$

$$r_{eq} = \frac{r}{n}$$

$$I = \frac{n\varepsilon}{nR + r}$$

★ Note :-

Factors on which internal resistance depends are :-

- ① Electrode surface area
- ② Electrode distance
- ③ Electrolyte concentration
- ④ Electrolyte Temperature
- ⑤ Electrolyte Nature.

V. Imp for Exam

★ Kirchhoff's Law :-

1. Kirchhoff's first law / Kirchhoff Current Law (KCL) :-

→ Based on law of conservation of charge.

→ According to this, at any junction the sum of current entering the junction is equal to the sum of currents leaving the junction.

$$\begin{array}{ccc}
 I_1 + I_2 & = & I_3 + I_4 + I_5 \\
 \downarrow & & \downarrow \\
 \text{Entering} & & \text{Leaving} \\
 \text{current} & & \text{current}
 \end{array}$$

$$\boxed{I_1 + I_2 - I_3 - I_4 - I_5 = 0} \rightarrow \text{at any junction total current is always zero.}$$

Note:-


- This law is valid for both open & closed circuit.
- If current is negative then consider direction opposite.

2. Kirchhoff's 2nd law / Kirchhoff Voltage law (KVL):-

- Based on law of conservation of energy.
- The algebraic sum of changes in potential around any closed loop involving resistors and cells is zero.

$$\boxed{\sum \Delta V = 0}$$

$$\boxed{V - IR_1 - IR_2 = 0}$$

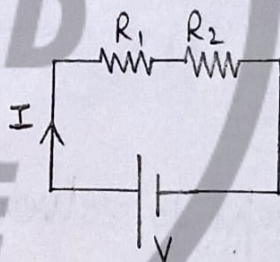

* Sign convention to apply Kirchhoff Law:-

• Sign for Potential:-



Higher Potential $\longrightarrow$ Low Potential
Potential drop.

$$\boxed{\Delta V = -ve}$$



Lower Potential $\longrightarrow$ High Potential
Potential gain

$$\boxed{\Delta V = +ve}$$

• Sign for cell :-

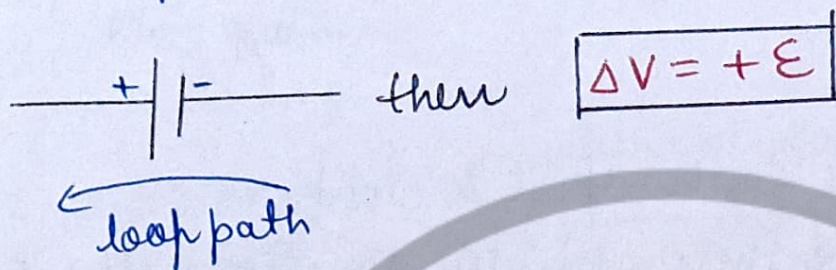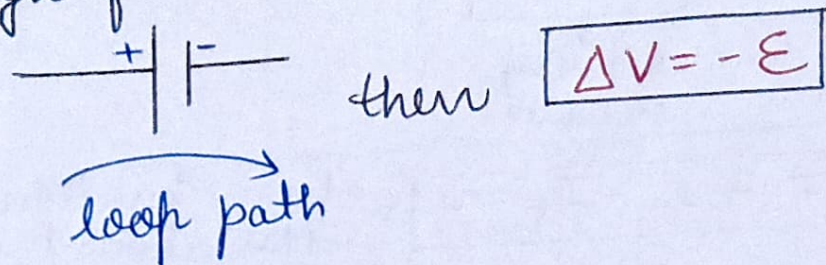


• Sign for Resistance :-

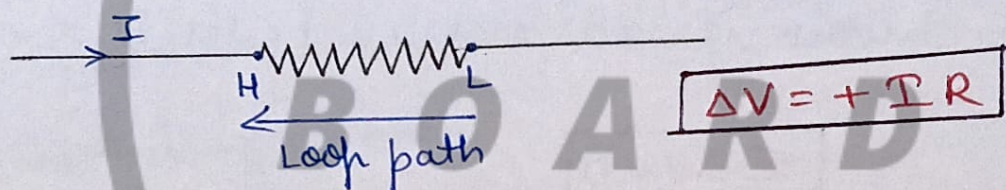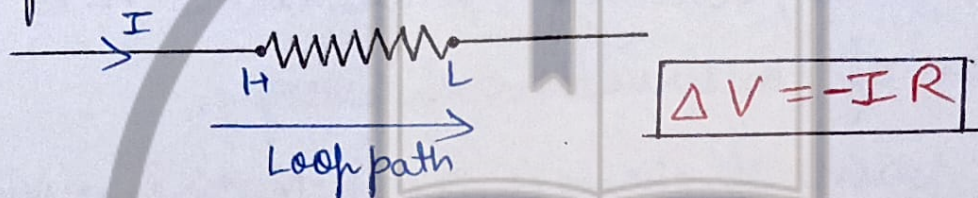


★ Steps to solve circuit By KVL :-

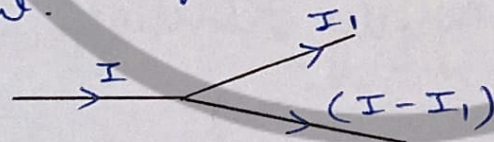① Draw the current from one or more cell and follow current law.



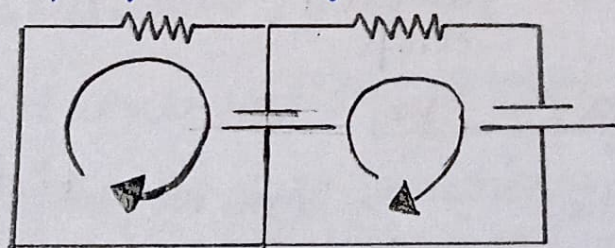② Choose a loop for every closed circuit.



May be clockwise or anticlockwise.

* Wheatstone Bridge :-

- Designed by C. F. Wheatstone.
- A special type of circuit containing four resistance, a galvanometer and a cell is called Wheatstone Bridge.
- It is used to find unknown resistance.

→ Its principle is that if $\boxed{\frac{P}{R} = \frac{Q}{S}}$ then $\boxed{I_g = 0}$

* Application :-


Meter Bridge and carry foster bridge follow this concept to find unknown resistance.

* Note :-

- If $P = Q = R = S$, then wheatstone bridge is sensitive.
- Internal resistance does not affect the value of unknown resistance.

* BOARD ZONE *

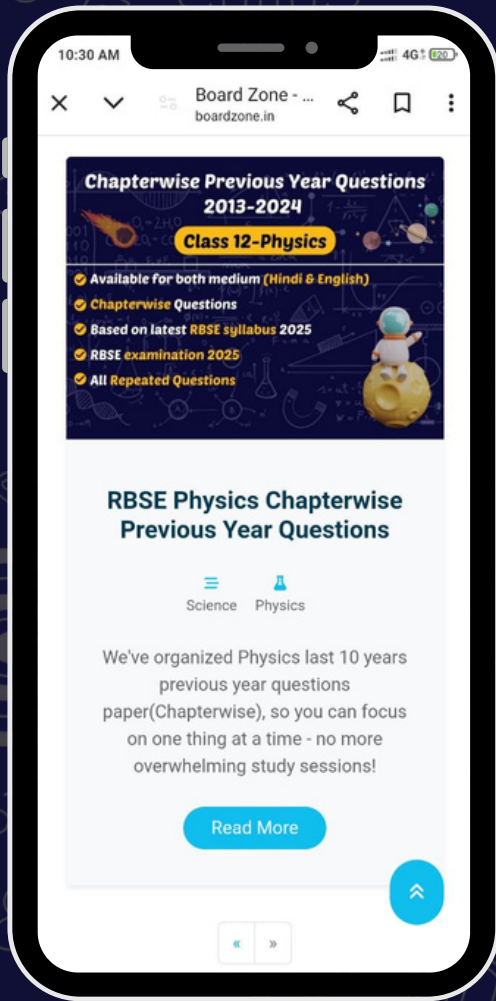राजस्थान बोर्ड की तैयारी के लिए आज ही हमारे
YouTube चैनल **Board Zone** और **Website**
BoardZone.in से जुड़ें।



- **CHAPTER-WISE PYQ**
- **HANDWRITTEN NOTES**
- **MCQ**
- **BLUE PRINT**
- **MODEL PAPER**
- **STRATEGY**
- **ETC**



921-6765-400

JOIN CHANNEL FOR FREE STUDY MATERIALS



YouTube



WhatsApp



Telegram